

# DESIGN NOTE

## Selecting the Right Power Inductor for DC/DC Converters

### INTRODUCTION

Buck and boost converters (Figure 1 and Figure 2) are common forms of DC/DC converters used in a wide variety of consumer automotive and industrial applications. Bourns® PQ Series power inductors are ideally suited for DC/DC converters operating at powers greater than 100 W. This Design Note provides a guide to selecting the right power inductor by providing design rules and key inductor values as well as the equations needed to determine peak and RMS currents.

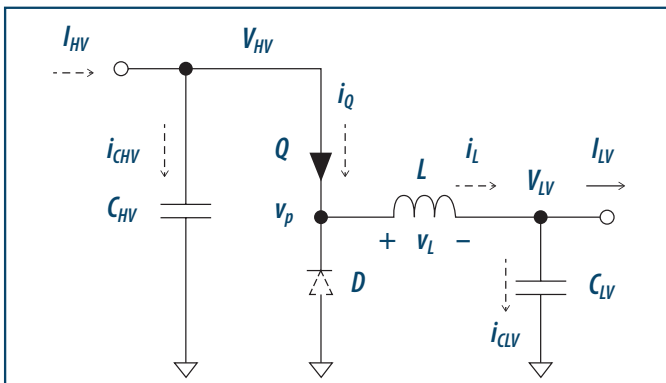


Figure 1 : Buck Converter

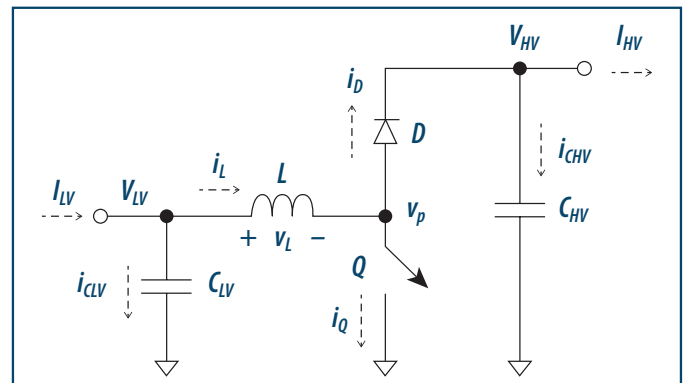


Figure 2 : Boost Converter

### KEY PARAMETERS REQUIRED

The following questions need to be answered in order to calculate the correct inductor value:

1. Operating frequency  $F_{sw}$  (kHz)
2. Output Power (watts)
3. Input and Output Voltages (volts)
4. Ripple Current in Inductor  $\Delta I_{pp}$  (amps)
5. Operating Mode (CCM, BCM, DCM)

### DESIGN STEPS

The calculations and steps below are necessary to determine the inductor that best meets the application requirements.

1. Calculate Average Current  $I_{out}$  (amps)
2. Calculate Duty Cycle  $D$  (Equations 1, 2, 8, 10)
3. Calculate the Inductance Value ( $\mu H$ ) (Equations 3, 9)
4. Calculate Inductor Max. Current (Amps) (Equations 4, 5)
5. Calculate Inductor RMS Current (Amps) (Equations 6,7)
6. Search for Suitable Inductor with Correct Inductance,  $I_{sat}$  and RMS Currents

# Selecting the Right Power Inductor for DC/DC Converters

## BUCK CONVERTER DESIGN EXAMPLE

The following inductor characteristics are typically required for a buck converter:

1.  $F_{sw} = 200$  kHz
2. Power = 264 watts
3.  $V_{in} = 48$  V<sub>dc</sub>,  $V_{out} = 12$  V<sub>dc</sub>
4. Ripple Current  $\Delta I_{pp} = 50$  A
5. Operating Mode = DCM (DCM2 = 0.1)

## CALCULATING A SOLUTION

Design Steps 1 through 6 are shown in Table 1 with the provided equations:

Calculate Average Current $I_{out}$	$I_{out} = \frac{264}{12} = 22 \text{ A}$			
Calculate Duty Cycle D (Equations 1, 2, 8, 10)	$D = \frac{12}{48(1 - 0.1)} = 0.3125$			
	$D_{cm1} = 1 - 0.3125 - 0.1 = 0.587$			
Calculate the Inductance Value (Equations 3, 9)	$L = \frac{(48 - 12) * 0.3125}{(50 * 200,000)} = 1.1 \mu\text{H}$			
Calculate Inductor Max. Current (Equations 4, 5)	$I_{max} = 50 \text{ A}$			
Calculate Inductor RMS current (Equations 6,7)	$I_{rms} = 50 \sqrt{\frac{0.3125 + 0.587}{3}} = 27.37 \text{ A}$			
The Optimum Power Inductor that Meets Inductance, $I_{sat}$ and RMS Current Requirements	Part Number	Inductance	RMS Current	Peak Current ( $I_{sat}$ )
	PQ2614BLA-1R5K	1.5 $\mu\text{H}$	30.0 A	100 A

Table 1

# Selecting the Right Power Inductor for DC/DC Converters

## BOURNS® PQ SERIES POWER INDUCTORS

Bourns designed the following features into the PQ Series power inductors to deliver considerable application benefits for high-power buck and boost converters.

Features	Benefits
Coil Made with Stamped Flat Wire	Low DC and AC Resistance
High Frequency Ferrite Core	<ul style="list-style-type: none"> <li>• Low Core Losses at High Frequency</li> <li>• High Permeability Material Requiring Fewer Turns than Iron Powder which means lower DC resistance</li> </ul>
Automated Production Line	High Quality
Available for Selection in LTpowerCAD®	Recognized by Leading Power Vendors

## SUMMARY OF EQUATIONS AND WAVEFORMS

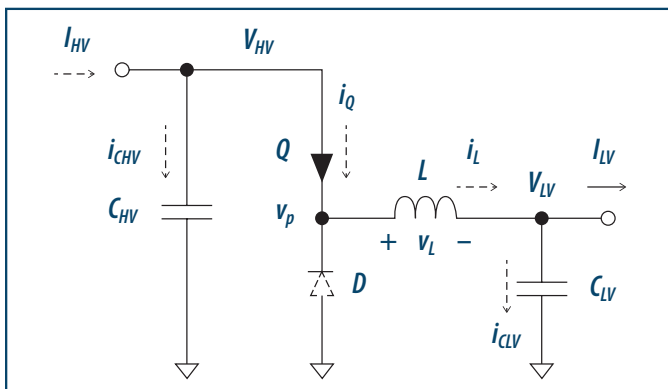


Figure 1 : Buck Converter

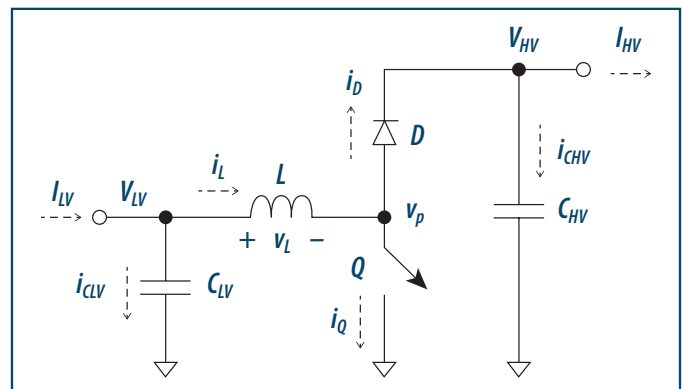


Figure 2 : Boost Converter

"LTpowerCAD" is a registered trademark of Analog Devices, Inc.

# Selecting the Right Power Inductor for DC/DC Converters

## SUMMARY OF EQUATIONS AND WAVEFORMS (CONTINUED)

Reference	Equation	Description	Waveform (if applicable)
1	$D = \frac{V_{out}}{V_{in}}$	Duty Cycle Buck in CCM and BCM	
2	$D = \frac{V_{out}}{V_{in}(1 - D_{cm2})}$	Duty Cycle Buck in DCM	<p>Inductor Voltage</p>
3	$L = \frac{(V_{in} - V_{out}) * D}{F_{sw} * \Delta I}$	Inductance	
4	$I_{Lmax} = I_o + \frac{\Delta I}{2}$	Max. Current CCM	<p>Inductor Current</p>
5	$I_{Lmax} = \Delta I$	Max. Current CCM and DCM	<p>Inductor Current</p>

# Selecting the Right Power Inductor for DC/DC Converters

## SUMMARY OF EQUATIONS AND WAVEFORMS (CONTINUED)

Reference	Equation	Description	Waveform (if applicable)
6	$I_{Lrms} = \sqrt{I_o^2 + \frac{\Delta I^2}{12}}$	RMS Current CCM and BCM	
7	$I_{Lrms} = \Delta I \sqrt{\frac{D + D_{cm1}}{3}}$	RMS Current Buck DCM and Boost DCM	
8	$D = 1 - \frac{V_{in}}{V_{out}}$	Duty Cycle Boost Converter	
9	$L = \frac{V_{in} D}{F_{sw} \Delta I}$	Inductance Boost Converter	
10	$D_{cm2} = 1 - \frac{V_{out} D}{V_{out} - V_{in}}$	DCM Duty Cycle	

[www.bourns.com](http://www.bourns.com)

**BOURNS®**

Americas: Tel +1-951-781-5500  
Email [americus@bourns.com](mailto:americus@bourns.com)

EMEA: Tel +36 88 885 877  
Email [eurocus@bourns.com](mailto:eurocus@bourns.com)

Asia-Pacific: Tel +886-2 256 241 17  
Email [asiacus@bourns.com](mailto:asiacus@bourns.com)